

CSE372

Digital Systems Organization and Design Lab

Prof. Milo Martin

Unit 1: Synthesizable Verilog


Hardware Description Languages (HDLs)

- Textual representation of a digital logic design
 - Easier to edit and revise than schematics
 - However, you still need to *think* in terms of schematics (pictures)
- HDLs are not “programming languages”
 - No, really. Even if they look like it, they are not.
 - **One of the most difficult conceptual leaps of this course**
- Similar development chain
 - Compiler: source code → assembly code → binary machine code
 - Synthesis tool: HDL source → gate-level specification → hardware

Hardware Description Languages (HDLs)

- Write “code” to describe hardware
 - Specify wires, gates, modules
 - Also hierarchical
- Pro: easier to edit and create; Con: more abstract
 
```
module mux2to1(S, A, B, O);  
  input S, A, B;  
  output O;  
  wire S_, AnS_, BnS;  
  
  not (S_, S);  
  and (AnS_, A, S_);  
  and (BnS, B, S);  
  or (O, AnS_, BnS);  
endmodule
```



Verilog HDL

- **Verilog**
 - One of two commonly-used HDLs
 - Verilog is a (surprisingly) big language
 - Lots of features for synthesis and simulation of hardware
- **We're going to learn a focused subset of Verilog**
 - Focus on synthesizable constructs
 - Focus on avoiding subtle synthesis errors
 - Use as an educational tool
 - Initially restrict some features to “build up” primitives
 - **Rule: if you haven't seen it in lecture, you can't use it**
 - **Ask me if you have any questions**

HDL History

- 1970s: First HDLs
- Late 1970s: VHDL
 - VHDL = VHSIC HDL = Very High Speed Integrated Circuit HDL
 - VHDL inspired by programming languages of the day (Ada)
- 1980s:
 - Verilog first introduced
 - Verilog inspired by the C programming language
 - VHDL standardized
- 1990s:
 - Verilog standardized (Verilog-1995 standard)
- 2000s:
 - Continued evolution (Verilog-2001 standard)
- Both VHDL and Verilog evolving, still in use today

Two Roles of HDL and Related Tools

- **#1: Specifying digital logic**
 - Specify the logic that appears in final design
 - Either
 - Translated automatically (called *synthesis*) or
 - Optimized manually (automatically checked for equivalence)
- **#2: Simulating and testing a design**
 - High-speed simulation is crucial for large designs
 - Many HDL *interpreters* optimized for speed
 - Testbench: code to test design, but not part of final design

Synthesis vs Simulation

- **HDLs have features for both synthesis and simulation**
 - E.g., simulation-only operations for error messages, reading files
 - Obviously, these can be simulated, but not synthesized into circuits
 - Also has constructs such as for-loops, while-loops, etc.
 - These are either un-synthesizable or (worse) synthesize poorly
- Trends: a moving target
 - Good: better synthesis tools for higher-level constructs
 - Bad: harder than ever to know what is synthesizable or not


Structural vs Behavioral HDL Constructs

- **Structural** constructs specify actual hardware structures
 - Low-level, direct correspondence to hardware
 - Primitive gates (e.g., and, or, not)
 - Hierarchical structures via modules
 - Analogous to programming software in assembly
- **Behavioral** constructs specify an operation on bits
 - High-level, more abstract
 - Specified via equations, e.g., $out = (a \& b) | c$
 - Statements, e.g., if-then-else
 - Analogous to programming software in C
- **Not all behavioral constructs are synthesizable**
 - Even higher-level, synthesize poorly or not at all (e.g., loops)
 - Perhaps analogous to programming in Perl, Python, Matlab, SQL

Verilog Structural vs Behavioral Example

Structural
 
```
module mux2to1(S, A, B, Out);
  input S, A, B;
  output Out;
  wire S_, AnS_, BnS;
  not (S_, S);
  and (AnS_, A, S_);
  and (BnS, B, S);
  or (Out, AnS_, BnS);
endmodule
```



Behavioral

```
module mux2to1(S, A, B, Out);
  input S, A, B;
  output Out;
  assign Out = (~S & A) | (S & B);
endmodule
```

Recall: Two Types of Digital Circuits

- **Combinational Logic**
 - Logic without state variables
 - Examples: adders, multiplexers, decoders, encoders
 - No clock involved
- **Sequential Logic**
 - Logic with state variables
 - State variables: latches, flip-flops, registers, memories
 - Clocked
 - State machines, multi-cycle arithmetic, processors
- **Today's lecture: Verilog for specifying combinational logic**
 - Sequential logic will be covered later
 - Focus on structural constructs with *limited* behavioral ones

Verilog Structural Primitives

- Gate-level
 - One-output boolean operators: **and**, **or**, **xor**, **nand**, **nor**, **xnor**
 - E.g., $C = A + B$

```
or (C, A, B);
```
 - E.g., $C = A + B + D$

```
or (C, A, B, D);
```
 - One-input operators: **not**, **buf**
 - E.g., $A = \text{not } Z$

```
not (A, Z);
```
 - E.g., $A = \text{not } Z, B = \text{not } Z$

```
not (A, B, Z);
```
 - Buf just replicates signals (can increase drive strength)
- Transistor-level primitives too
 - Will not use

Three Module Components

- Interface specification

```
module mux2to1(S, A, B, O);
  input S, A, B;
  output O;
```

 - Can also have **inout**: bidirectional wire (we will not need)
- Alternative: Verilog 2001 interface specification

```
module mux2to1(input S, A, B, output O);
```
- Declarations
 - Internal wires, i.e., "local" variables
 - Wires also known as "nets" or "signals"


```
wire S_, AnS_, BnS;
```
- Implementation: primitive and module instantiations

```
and (AnS_, A, S_);
```

Verilog Module Example

```
module mux2to1(S, A, B, O);
  input S, A, B;
  output O;
  wire S_, AnS_, BnS;

   not (S_, S);
  and (AnS_, A, S_);
  and (BnS, B, S);
  or (O, AnS_, BnS);
endmodule
```



Hierarchical Verilog Example

- Build up more complex modules using simpler modules
- Example: 4-bit wide mux from four 1-bit muxes
 - Again, just “drawing” boxes and wires

```
module mux2to1_4(Sel, A, B, O);
  input [3:0] A;
  input [3:0] B;
  input Sel;
  output [3:0] O;

  mux2to1 mux0 (Sel, A[0], B[0], O[0]);
  mux2to1 mux1 (Sel, A[1], B[1], O[1]);
  mux2to1 mux2 (Sel, A[2], B[2], O[2]);
  mux2to1 mux3 (Sel, A[3], B[3], O[3]);
endmodule
```

Connections by Name

- Can (should) specify module connections by name
 - Helps keep the bugs away
 - Example

```
mux2to1 mux0 (.S(Sel), .A(A[0]), .B(B[0]), .O(O[0]));
```
 - Also, order doesn't matter

```
mux2to1 mux1 (.A(A[1]), .B(B[1]), .O(O[1]), .S(Sel));
```

Vectors of Wires

- Wire vectors:

```
wire [7:0] W1; // 8 bits, w1[7] is MSB
wire [0:7] W2; // 8 bits, w2[0] is MSB
```

 - Also called “arrays” or “busses”
- Operations
 - Bit select: `W1[3]`
 - Range select: `W1[3:2]`
 - Concatenate: `{<expr>[,<expr>]*}`

```
vec = {x, y, z};
{carry, sum} = vec[0:1];
```
 - e.g., swap high and low-order bytes of 16-bit vector

```
wire [15:0] w1, w2;
assign w2 = {w1[7:0], w1[15:8]}
```

Wire and Vector Assignment

- Wire assignment: “continuous assignment”
 - Connect combinational logic block or other wire to wire input
 - **Order of statements not important**, executed totally in parallel
 - When right-hand-side changes, it is re-evaluated and re-assigned
 - Designated by the keyword **assign**

```
wire c;  
assign c = a | b;  
wire c = a | b;    // same thing
```

Operators

- Operators similar to C or Java
- On wires:
 - & (and), | (or), ~ (not), ^ (xor)
- On vectors:
 - &, |, ~, ^ (bit-wise operation on all wires in vector)
 - E.g., assign vec1 = vec2 & vec3;
 - &, |, ^ (reduction on the vector)
 - E.g., assign wire1 = | vec1;
 - Even ==, != (comparisons) +, -, * (arithmetic), <<, >> (shifts)
 - But you can't use these, yet. Can you guess why?
 - Note: use with care, assume unsigned numbers
 - Verilog 2001: signed vs unsigned vectors, >>> operator
- Can be arbitrarily nested: (a & ~b) | c

Conditional Operator

- Verilog supports the ?: conditional operator
 - Almost never useful in C (in my opinion)
 - Much more useful in Verilog

- Examples:

```
assign out = S ? B : A;  
  
assign out = sel == 2'b00 ? a :  
             sel == 2'b01 ? b :  
             sel == 2'b10 ? c :  
             sel == 2'b11 ? d : 1'b0;
```

- What do these do?

Miscellaneous

- Operators and expressions can be used with modules
 - `mux2to1 mux0 (cond1 & cond2, a, b, out);`
- C/Java style comments
 - // comment until end of line
 - /* comment between markers */
- All variable names are case sensitive
- Constants:
 - assign x = 3'b011
 - The “3” is the number of bits
 - The “b” means “binary” - “h” for hex, “d” for decimal
 - The “011” are the digits (in binary in this case)

Arrays of Modules

- Verilog also supports arrays of module instances
 - Well, at least some Verilog tools
 - Support for this feature varies

```
module mux2to1_4(Sel, A, B, O);
    input [3:0] A;
    input [3:0] B;
    input Sel;
    output [3:0] O;

    mux2to1 mux0[3:0] (Sel, A, B, O);
endmodule
```

Parameters

- Allow per-instantiation module parameters
 - Use "parameter" statement
- modname #(10, 20, 30) instname(in1, out1);
- Example:

```
module mux2to1_N(Sel, A, B, O);
    parameter N = 1;
    input [N-1:0] A;
    input [N-1:0] B;
    input Sel;
    output [N-1:0] O;
    mux2to1 mux0[N-1:0] (Sel, A, B, O);
endmodule

...
Mux2to1_N #(4) mux1 (S, in1, in2, out)
```

Last Multiplexer Example

- Using conditional operator

```
module mux2to1_N(Sel, A, B, Out);
    parameter N = 1;
    input [N-1:0] A;
    input [N-1:0] B;
    input Sel;
    output [N-1:0] Out;
    assign Out = Sel ? B : A;
endmodule
```

Verilog Pre-Processor

- Like the C pre-processor
 - But uses ` (back-tick) instead of #
 - Constants: `define
 - No parameterized macros
 - Use ` before expanding constant macro
 - Conditional compilation: `ifdef, `endif
 - File inclusion: `include
- Parameter vs `define
 - Parameter only for "per instance" constants
 - `define for "global" constants

Common Errors

- Tools are from a less gentle time
 - More like C, less like Java
 - Assume that you mean what you say
- Common errors:
 - Not assigning a wire a value
 - Assigning a wire a value more than once
 - Implicit wire declarations (default to type "wire")
 - Disable by adding the following to the file:
 - ``default_nettype none`
 - Does not work with ModelSim
- Avoid names such as:
 - clock, clk, power, pwr, ground, gnd, vdd, vcc, init, reset, rst
 - Some of these are "special" and will silently cause errors

Additional Verilog Resources

- Elements of Logic Design Style by Shing Kong, 2001
 - Dos, do-nots, tips
 - <http://www.cis.upenn.edu/~milom/elements-of-logic-design-style/>
- Verilog HDL Synthesis: A Practical Primer
 - By J. Bhasker, 1998
 - To the point (<200 pages)
- Advanced Digital Design with the Verilog HDL
 - By Michael D. Ciletti, 2003
 - Verilog plus lots of digital logic design (~1000 pages)
- Verilog tutorial on CD from "Computer Org. and Design"

CSE372 Digital Systems Organization and Design Lab

Prof. Milo Martin

Unit 1: Synthesizable Verilog (continued)

Lab 1 - ALU (Arithmetic/Logical Unit)

- Task: design an ALU for a P37X CPU
- Ten operations:
 - Addition, subtraction
 - Multiplication
 - And, or, not, xor
 - Shift left, logical shift right, arithmetic shift right
- The different adder implementations
 - Ripple-carry
 - Two carry-select adders
- Pay close attention in CSE371 lecture this week!

Aside: Honors Points

- Goals:
 - Make the labs accessible to all
 - Challenge those that want more
- So, I'm trying something different
 - Again, experimental
- Labs will have two types of "points"
 - "Normal" - standard labs
 - "Honors" - above and beyond
- Normal points
 - Get all the normal points -> A- in the class
- Honors points
 - Will distinguish the A- from A and A+
 - May bump others a third of a letter grade
- Examples: fast adders (lab 1), advanced pipelines

Aside: Due Dates and Late Days

- Normal due dates
 - Lab demos are on Fridays
 - Lab write-ups are due on Mondays (at **start** of class)
- I'll give you two "late credits" for the semester
 - Used for emergencies, sickness, travel, etc.
 - Otherwise, no late assignments accepted
- Impact of using a "late credit"
 - Demo moved from Friday to Monday
 - Lab write-up moved from Monday to Wednesday (in TA lab hours)
 - No "honors points" for these late assignments

Repeated Signals

- Last time we discussed vector concatenation

```
assign vec = {x, y, z};
```
- Can also repeat a signal n times

```
assign vec = {16{x}}; // 16 copies of x
```
- Example uses (what does this do?):

```
wire [7:0] out;  
wire [3:0] A;  
assign out = {{4{0}}, A[3:0]};
```
- What about this?


```
assign out = {{4{A[3]}}, A[3:0]};
```

FYI: Non-binary Hardware Values

- A hardware signal can have four values
 - **0**, **1**
 - **x**: don't know, don't care
 - **z**: high-impedance (no current flowing)
- Uses for "x"
 - Tells synthesis tool you don't care
 - Synthesis tool makes the most convenient circuit (fast, small)
 - Use with care, leads to synthesis dependent operation
- Uses for "z"
 - Tri-state devices drive a zero, one, or nothing (z)
 - Many tri-states drive the same wire, all but one must be "z"
 - Makes some circuits very fast
 - Example: multiplexer
 - Why Verilog allows multiple assignments to same wire.

Simulation

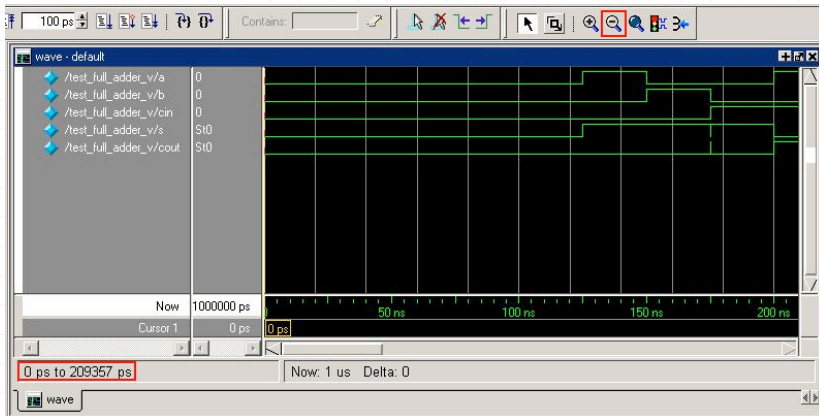- Used to test and debug our designs
- Graphical output via waveforms



CSE 372 (Martin): Synthesizable Verilog

33

Levels of Simulation

- Functional (or Behavioral) Simulation
 - Simulates Verilog abstractly
 - No timing information, can't detect timing "bugs"
- Post-synthesis Timing Simulation
 - Simulating devices generated via synthesis
 - Gates, transistors, FPGA logical units (LUTs)
 - No interconnect delay
 - Not all internal signals may still exist
 - Synthesis might have optimized or changed the design
 - Slower
- Layout Timing Simulation
 - After synthesis, the tool "places and routes" the logic blocks
 - Includes all sources of delay
 - Even slower

CSE 372 (Martin): Synthesizable Verilog

34

Sequential Logic in Verilog

- How do we specify state-holding constructs in Verilog?


```
module dff (Clock, D, WE, Reset, Q);
  input Clock, D, WE, Reset;
  output Q;
  reg Q;
  always @(posedge Clock)
  begin
    if (Reset)
      Q = 1'b0;
    else if (WE)
      Q = D;
  end
endmodule
```

CSE 372 (Martin): Synthesizable Verilog

35

Designing Sequential Logic

 - CSE372 design rule: separate comb. logic from sequential state elements
 - Not enforced by Verilog, but a very good idea
 - Possible exceptions: counters, shift registers
- We'll give you a 1-bit flip-flop module (see previous slide)
 - Edge-triggered, not a latch
 - Use it to build a n-bit register
- Example use: state machine



CSE 372 (Martin): Synthesizable Verilog

36

Clocks Signals

- Clocks signals are not normal signals
- Travel on dedicated "clock" wires
 - Reach all parts of the chip
 - Special "low-skew" routing
- Ramifications:
 - Never do logic operations on the clocks
 - If you want to add a "write enable" to a flip-flop:
 - Use a mux to route the old value back into it
 - Do not just "and" the write-enable signal with the clock!
- Messing with the clock can cause a errors
 - Often can only be found using timing simulation