

CSE372

Digital Systems Organization and Design Lab

Prof. Milo Martin

Unit 2: Field Programmable Gate Arrays (FPGAs)


Announcements

- Lab 1 due in one week
 - Questions/comments?
 - Testbench coming soon (according to the TAs)
- Today's lecture:
 - How FPGAs work


Field Programmable Gate Array (FPGA)

- An alternative to a "custom" design
 - A high-end custom design "mask set" is expensive (millions of \$!)
- Advantages
 - Simplicity of gate-level design (no transistor-level design)
 - Fast time-to-market
 - No manufacturing delay
 - Can fix design errors over time (more like software)
- Disadvantages
 - Expensive: unit cost is higher
 - Inefficient: slower and more power hungry
- Result: good for low-volume or initial designs

Early Programmable Logic Device...

 


Modern FPGA: Xilinx Vertex II

 

CSE 372 (Martin): FPGAs

5

For Comparison: FGPA vs Pentium 4

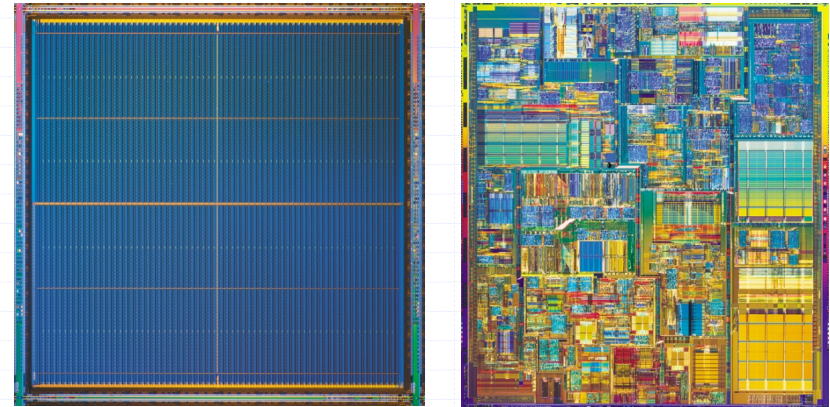

Not to scale

CSE 372 (Martin): FPGAs

6

FPGA Design Flow


- Synthesis
 - Break design into well-define logic blocks
 - Examples:
 - 2-input gates
 - Only NANDs
 - Limited set of "standard cells" with three-inputs, one output
- Place and route
 - Custom: position the devices and wires that connect them
 - FPGA: configure logic blocks and interconnect
- Goals:
 - Reduce latency (performance)
 - Reduce area (cost)
 - Reduce power (performance and/or cost)

CSE 372 (Martin): FPGAs

7

Review: Logical Completeness

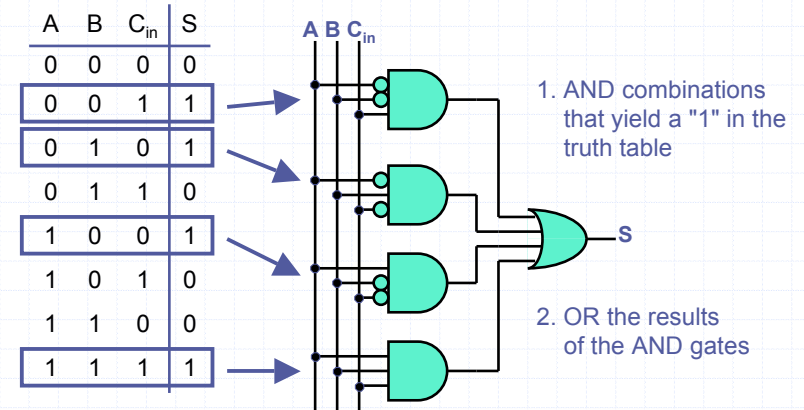- AND, OR, NOT can implement ANY truth table



Mechanical process, but many optimizations


CSE 372 (Martin): FPGAs

8

Our Old Friend, The Full Adder

- Add two bits and carry-in produce one-bit sum and carry-out

A	B	C _{in}	S	C _{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 


A Better Full Adder


```

module full_adder(s, cout, a, b, cin);
    output s, cout;
    input a, b, cin;

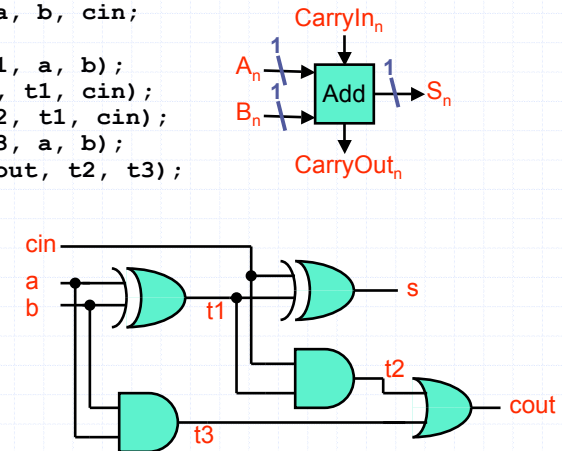    xor (t1, a, b);
    xor (s, t1, cin);
    and (t2, t1, cin);
    and (t3, a, b);
    or (cout, t2, t3);
endmodule
    
```





A Simple (Fake) FPGA Substrate

 


How Do We "Route" Signals?

  - Switch matrix
 - Each junction has 6 "switches"
 - Each switch is a pass gate
- Programming
 - Each pass gate controlled by 1-bit flip-flop
 - 0/1 value of flip-flop set at configuration
- Programmable "interconnect"
 - Allows for arbitrary routing of signals
 - Each segment adds delay
 - Takes up lots of chip area




On-Chip Wires

 

©IBM


More Wires

 

©IBM


IBM CMOS7, 6 layers of copper wiring

Configure This As a Full Adder

 

A Better FPGA

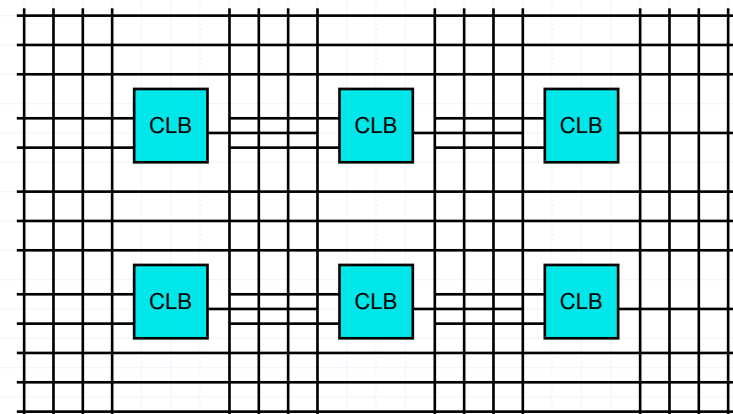- Replace gates with general "CLB"
 - Combinational logic block



Combinational Logic Block

- Simple example CLB
 - Configure as any two-input gate
 - Use 4-bit RAM to implement function
 - LUT - Lookup Table
 - Simple lookup operation
- Add sequential state
 - Add a latch/flipflop or two

A Standard Xilinx CLB

- Two 4-input LUTs
 - Any 4-input function
 - Limited 5-input functions
- Two flip-flops
- Fast carry logic (direct connect from adjacent CLBs)
- LUTs can be configured as RAM:
 - 2x16 bit or 1x32 bit, single ported
 - 1x16 bit dual ported
- Routing
 - Short and long wires (skip some CLBs)
 - Clocks have dedicated wires
- Also has IOBs (input/output blocks)
 - Specialized for off-chip signals, one per pin on package

The Xilinx 4000 CLB

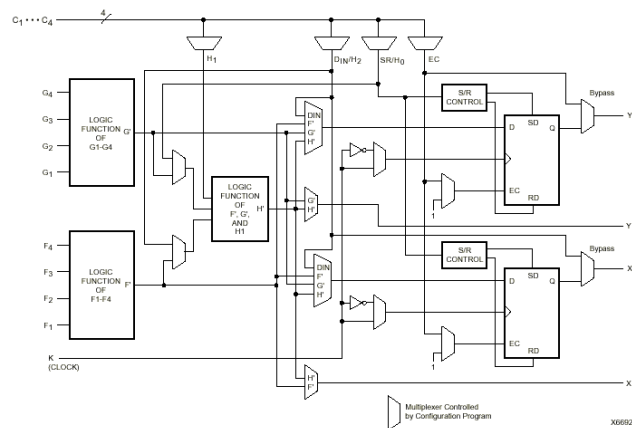


Figure 1: Simplified Block Diagram of XC4000 Series CLB (RAM and Carry Logic functions not shown)

Two 4-input functions, registered output

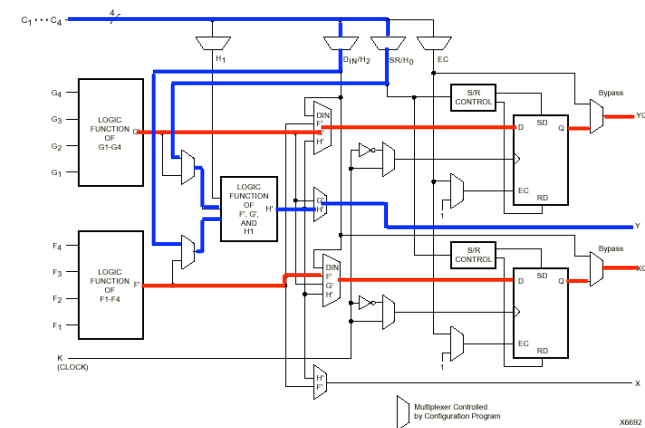


Figure 1: Simplified Block Diagram of XC4000 Series CLB (RAM and Carry Logic functions not shown)

5-input function, combinational output

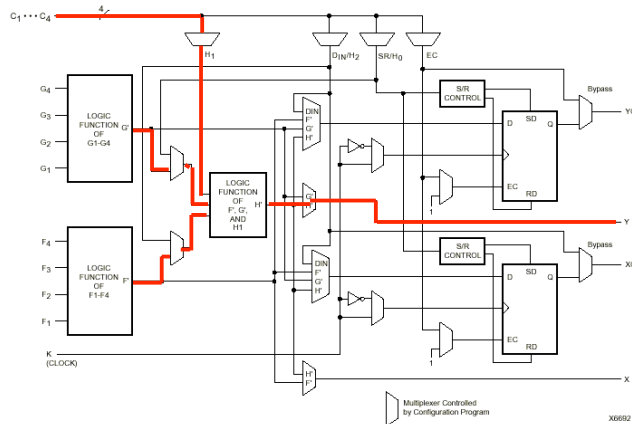


Figure 1: Simplified Block Diagram of XC4000 Series CLB (RAM and Carry Logic functions not shown)

CLB Used as RAM


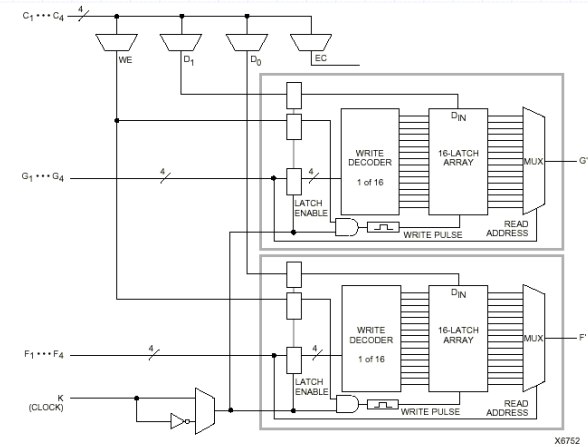


Figure 4: 16x2 (or 16x1) Edge-Triggered Single-Port RAM

Fast Carry Logic

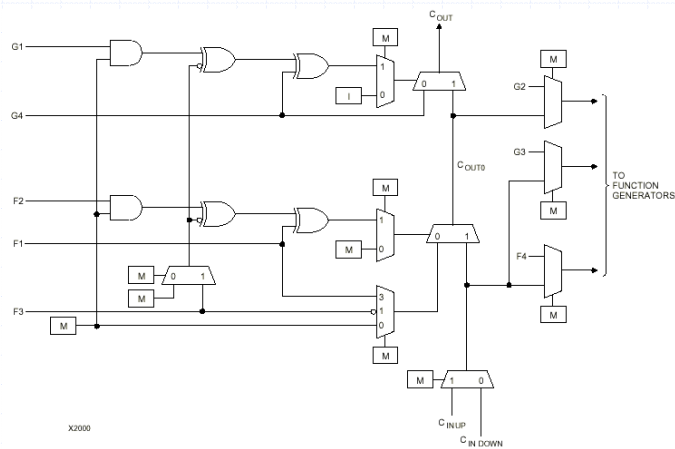

Xilinx 4000 Interconnect

 


Figure 28: Single- and Double-Length Lines, with Programmable Switch Matrices (PSMs)

Switch Matrix


 


Figure 26: Programmable Switch Matrix (PSM)

Xilinx 4000 Interconnect Details

 

FPGA Design Issues

- How large should a CLB be?
 - How many inputs?
 - How much logic and state?
 - Example: two full-adders plus two latches in each Xilinx CLB
 - N-bit counter uses $N/2$ CLBs
- Routing resources
 - Faster, better routing
- Other imbedded hardware structures
 - RAM blocks
 - Multipliers
 - Processors


Our FPGAs: Virtex-2 Pro XC2VP30

- Virtex-2 Pro
 - More powerful CLBs
 - More routing resources
 - Embedded PowerPC core
- XC2VP30
 - 30,816 CLBs
 - 136 18-bit multipliers
 - 2,448 Kbits of block RAM
 - Two PowerPC processors
 - 400+ pins

FPGA vs Custom Designs

- Downside of configurability
 - Wires are much slower on FPGAs
 - Logic is much slower on FPGAs
- However, FPGAs are “real” logic (not software)
 - Great for our prototyping
- “Synthesis to chip” an option (\$\$\$)
 - Standard cell design
 - Hard coded, but based on synthesis design flow
 - Not as good as “full custom” as used by Intel, AMD, IBM

FPGA vs Custom Designs

 

Not to scale